


Cairo University
Faculty of engineering
Dept. of Electronics and Electrical Communications
Second Year

ELECTRONICS
ELC 2020
RF amplifier

Answer Sheet

ID	Section	Name
9220473	2	عبدالرحمن محمد صلاح الدين أبو هندي
9220640	3	محمد إبراهيم يوسف الدميري


	Expression	Calculated Values	Simulated Values
BE Junction Voltage	V_{BE}	0.7 V	0.792 V
Base Current	$I_B = \frac{V_{BB} - V_{BE}}{R_{BB} - (\beta + 1)R_E}$ $V_{BB} = V_{CC} \frac{R_3}{R_2 + R_3}, R_{BB} = R_2 R_3$	22.096 μA	20.519 μA
Collector Current	βI_B	2.2096 mA	2.0519 mA
Collector Voltage	$V_{CC} - I_C * R_1$	11.9779 V	11.9794 v
Load Impedance At Resonance	$Z_{res} = \frac{L_1}{R_1 C_2}$	0.15625 MΩ	0.155 MΩ
Quality Factor	$Q = \frac{Z_{res}}{X_L}$	125	121.541
Center Frequency	$F_c = \frac{1}{2\pi\sqrt{L_1 C_2}}$	1.59154 MHZ	1.5922 MHZ
BW	$\frac{F_c}{Q}$	12732.32 HZ	13000 HZ

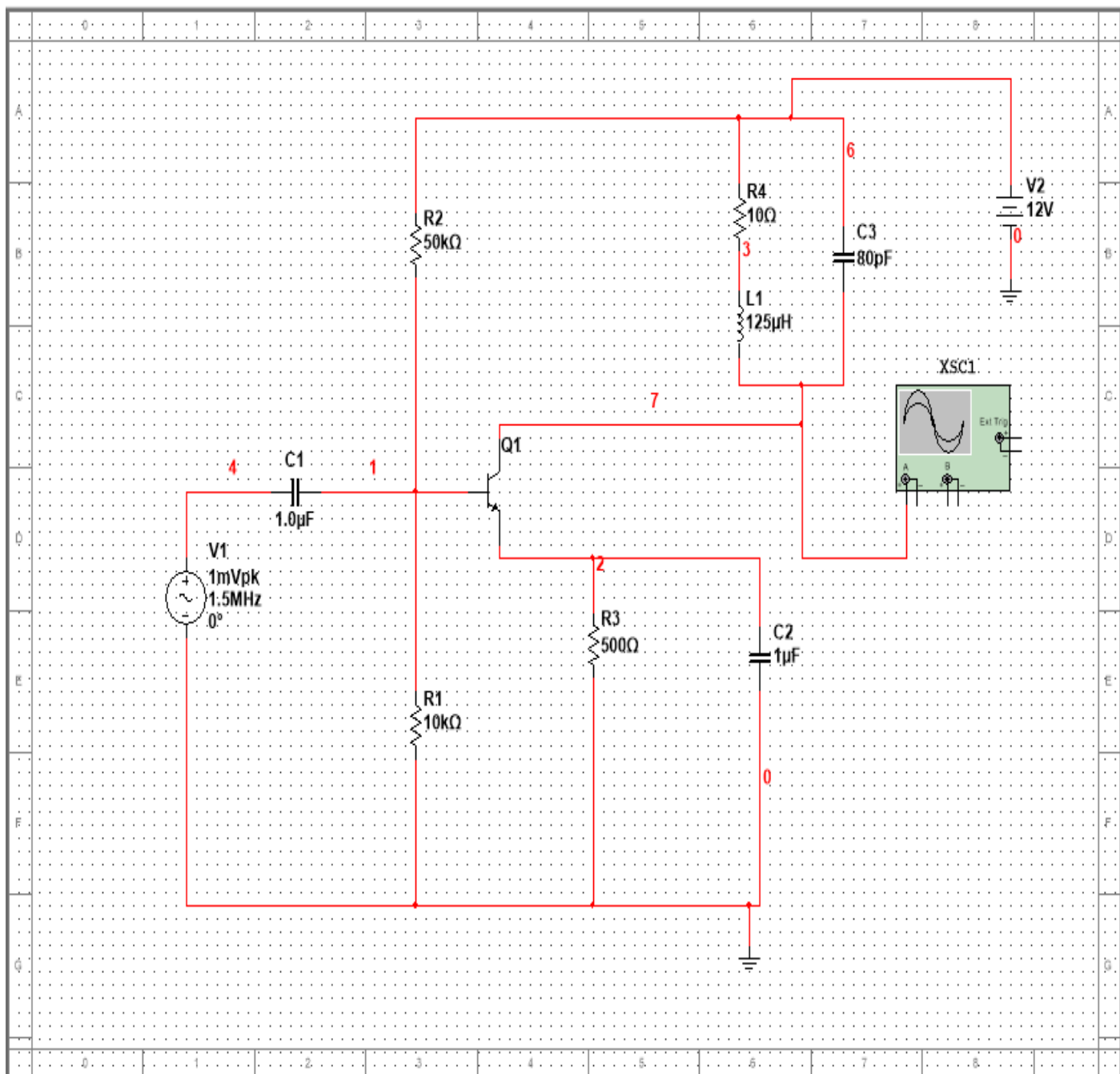


The simulated Circuit

	Simualtion																																
1.BE Junction Voltage 2.Collector Voltage 3.Base Current 4.Collector Current	<table><thead><tr><th></th><th>Variable</th><th>Operating point value</th></tr></thead><tbody><tr><td>1</td><td>V(1)-V(2)</td><td>792.79868 m</td></tr><tr><td>2</td><td>V(7)</td><td>11.97948</td></tr><tr><td>3</td><td>I(Q1[IB])</td><td>20.51899 u</td></tr><tr><td>4</td><td>I(Q1[IC])</td><td>2.05190 m</td></tr></tbody></table>		Variable	Operating point value	1	V(1)-V(2)	792.79868 m	2	V(7)	11.97948	3	I(Q1[IB])	20.51899 u	4	I(Q1[IC])	2.05190 m																	
	Variable	Operating point value																															
1	V(1)-V(2)	792.79868 m																															
2	V(7)	11.97948																															
3	I(Q1[IB])	20.51899 u																															
4	I(Q1[IC])	2.05190 m																															
Load Impedance At Resonance	<p>We calculated the load impedance at resonance by dividing the voltage at center frequency by the current at the center frequency.</p> <div><div><p>Cursor</p><p>V (7)</p><table><tbody><tr><td>x1</td><td>1.5729M</td></tr><tr><td>y1</td><td>4.0047k</td></tr><tr><td>x2</td><td>1.5922M</td></tr><tr><td>y2</td><td>12.3279k</td></tr><tr><td>dx</td><td>19.3207k</td></tr><tr><td>dy</td><td>8.3231k</td></tr><tr><td>dy/dx</td><td>430.7893m</td></tr><tr><td>1/dx</td><td>51.7580u</td></tr></tbody></table></div><div><p>Cursor</p><p>I (Q1 [IC])</p><table><tbody><tr><td>x1</td><td>295.2608k</td></tr><tr><td>y1</td><td>79.2546m</td></tr><tr><td>x2</td><td>1.5919M</td></tr><tr><td>y2</td><td>79.3309m</td></tr><tr><td>dx</td><td>1.2966M</td></tr><tr><td>dy</td><td>76.3000u</td></tr><tr><td>dy/dx</td><td>58.8459p</td></tr><tr><td>1/dx</td><td>771.2441n</td></tr></tbody></table></div></div> <p>Load Impedance = $\frac{12.3279 \text{ kV}}{79.3309 \text{ mA}} = 155400 \Omega = 0.1554 \text{ k}\Omega$</p>	x1	1.5729M	y1	4.0047k	x2	1.5922M	y2	12.3279k	dx	19.3207k	dy	8.3231k	dy/dx	430.7893m	1/dx	51.7580u	x1	295.2608k	y1	79.2546m	x2	1.5919M	y2	79.3309m	dx	1.2966M	dy	76.3000u	dy/dx	58.8459p	1/dx	771.2441n
x1	1.5729M																																
y1	4.0047k																																
x2	1.5922M																																
y2	12.3279k																																
dx	19.3207k																																
dy	8.3231k																																
dy/dx	430.7893m																																
1/dx	51.7580u																																
x1	295.2608k																																
y1	79.2546m																																
x2	1.5919M																																
y2	79.3309m																																
dx	1.2966M																																
dy	76.3000u																																
dy/dx	58.8459p																																
1/dx	771.2441n																																
Quality Factor	<p>Quality Factor is calculated by dividing the simulated center frequency by the bandwidth.</p>																																


Center
Frequency

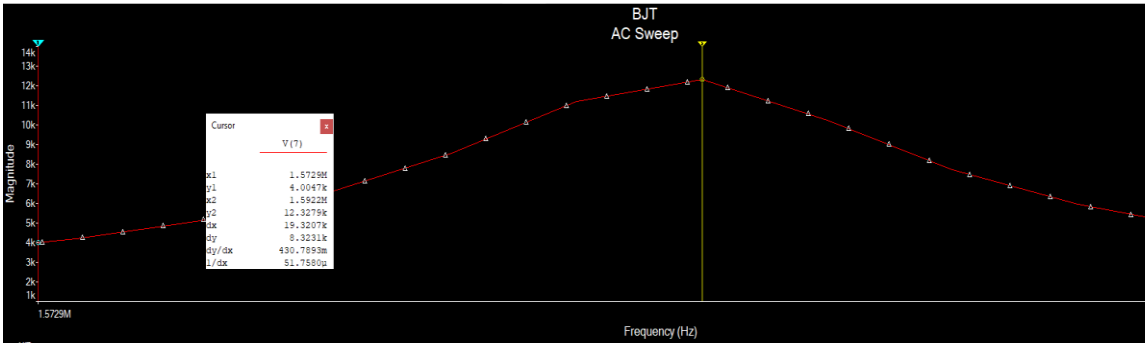

BW

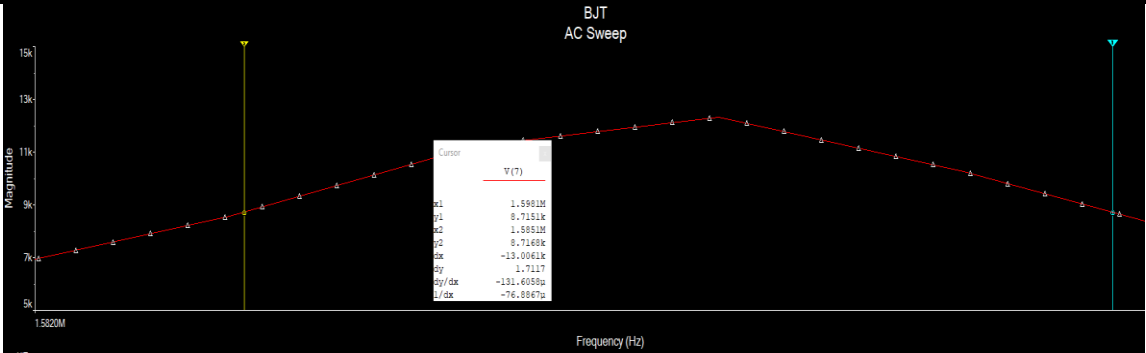


Band width from linear scale

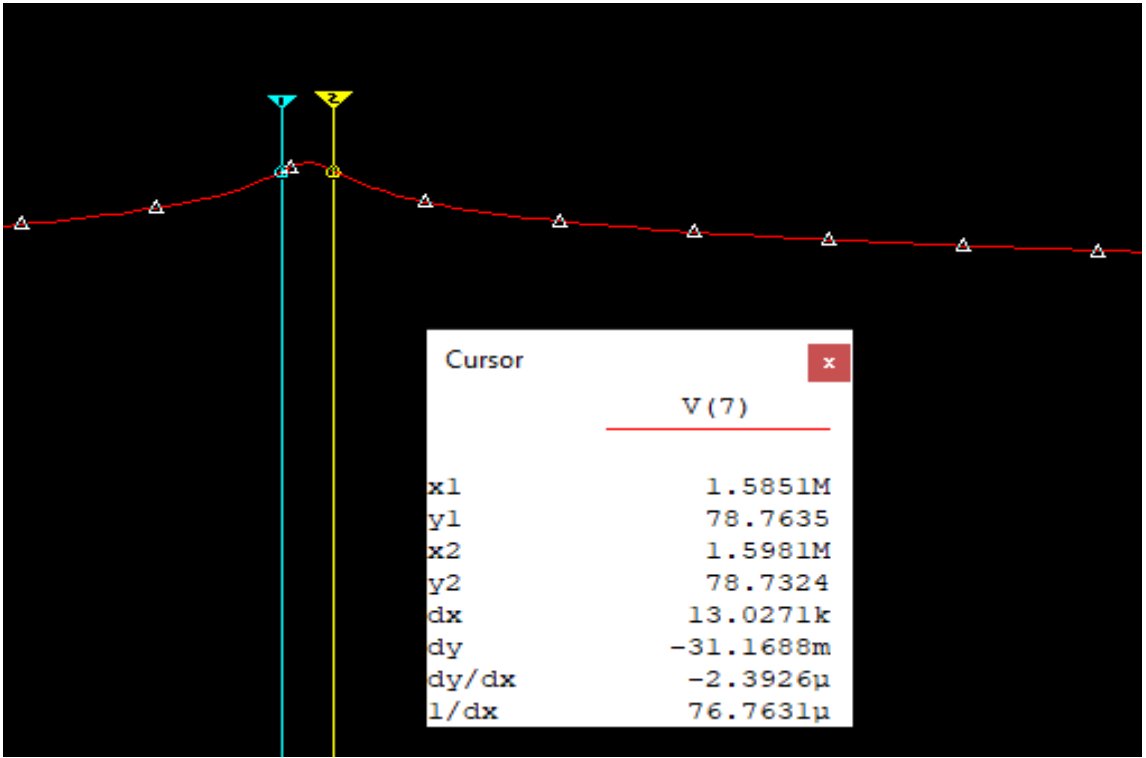


Band width from decibel scale

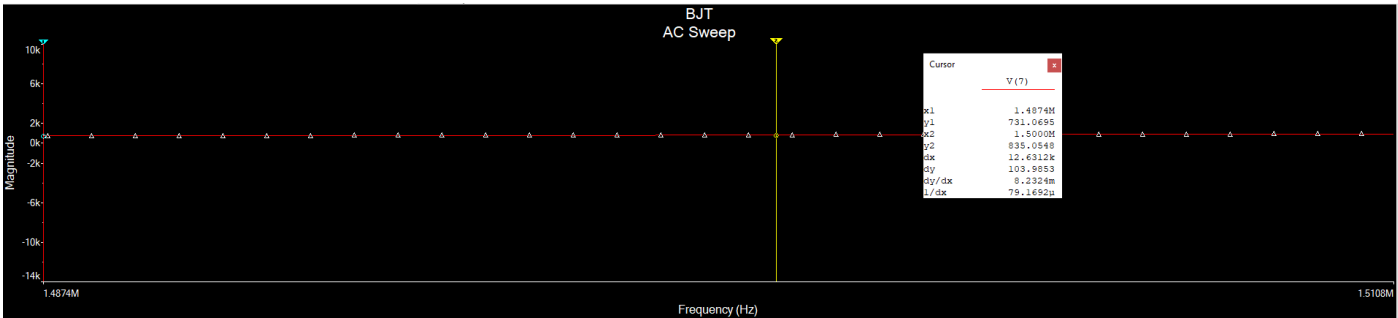Q2) The gain at 1.5MHz = 58.43 DB= 835.05 V/V




Gain

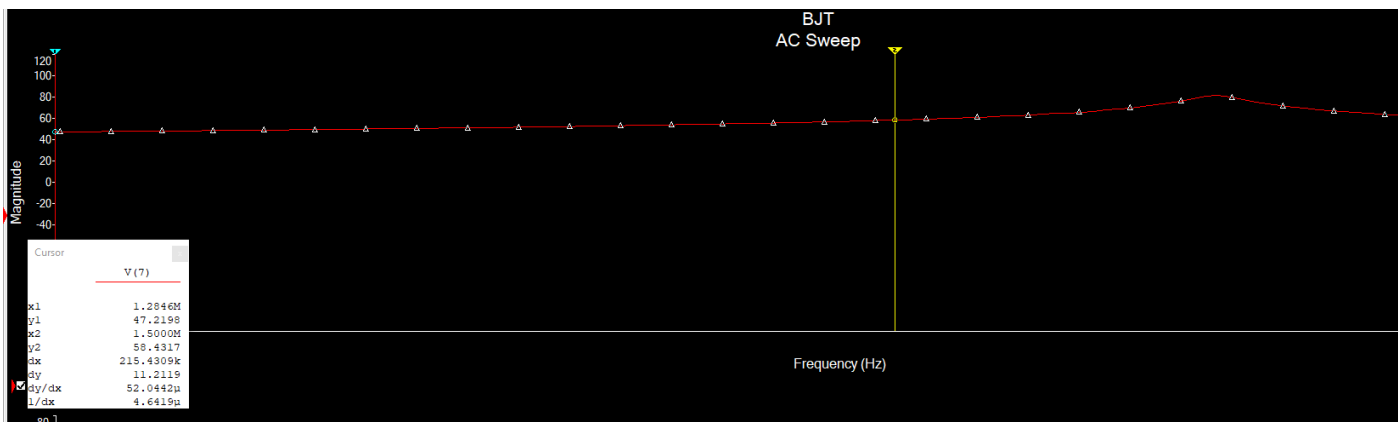

Decibel gain

Q3)

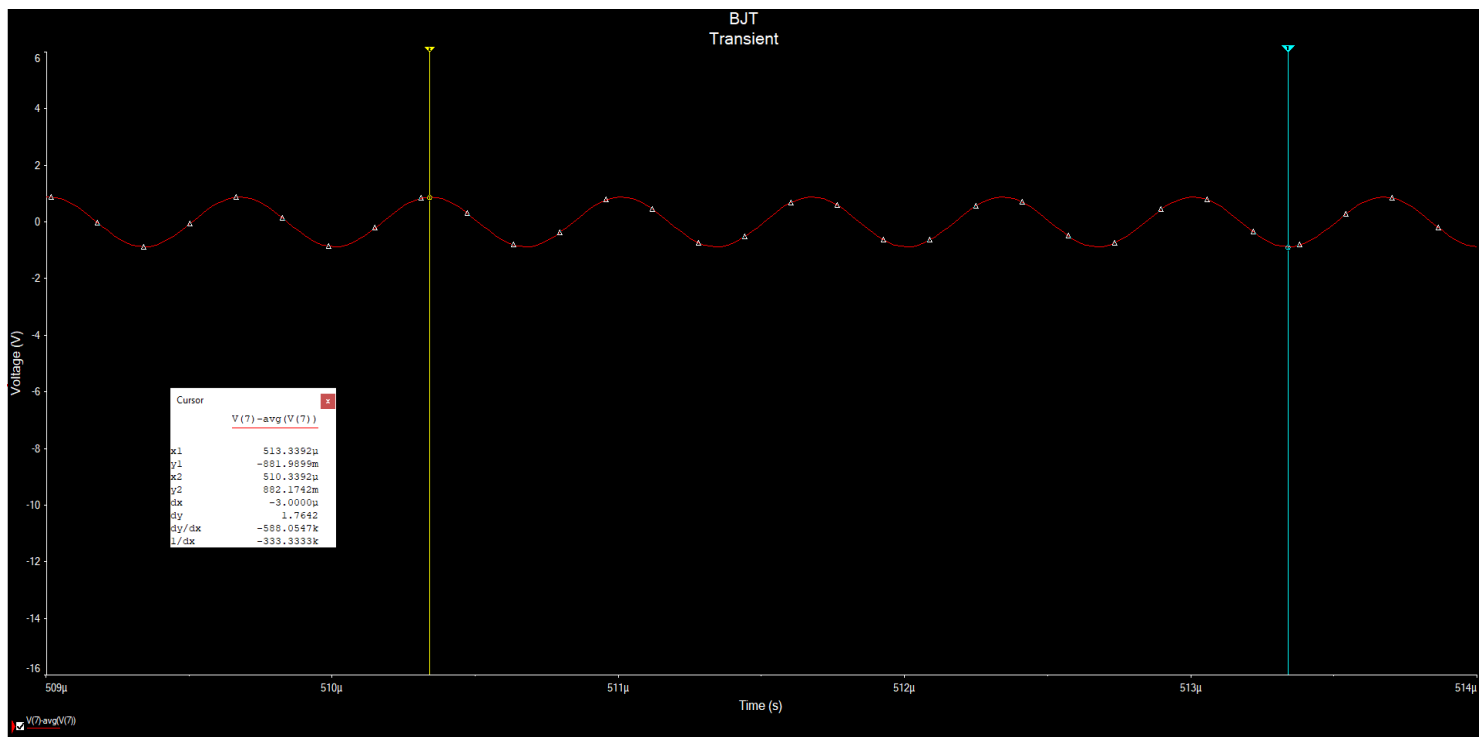

- The Amplitude at 1.5MHz = 882 mV.
- The Expected Value from AC Simulation = 835.05 mV.